
When measuring a capacitor via a Keysight LCR meter, what is the best circuit mode, Cs or Cp?

Technical Support Knowledge Center Open

Notices

© Keysight Technologies Incorporated, 2002-2023

1400 Fountaingrove Pkwy., Santa Rosa, CA 95403-1738, United States All rights reserved.

No part of this documentation may be reproduced in any form or by any means (including electronic storage and retrieval or translation into a foreign language) without prior agreement and written consent from Keysight Technologies, Inc. as governed by United States and international copyright laws.

Restricted Rights Legend

If software is for use in the performance of a U.S. Government prime contract or subcontract, Software is delivered and licensed as "Commercial computer software" as defined in DFAR 252.227-7014 (June 1995), or as a "commercial item" as defined in FAR 2.101(a) or as "Restricted computer software" as defined in FAR 52.227-19 (June 1987) or any equivalent agency regulation or contract clause.

Use, duplication or disclosure of Software is subject to Keysight Technologies' standard commercial license terms, and non-DOD Departments and Agencies of the U.S. Government will receive no greater than Restricted Rights as defined in FAR 52.227-19(c)(1-2) (June 1987). U.S. Government users will receive no greater than Limited Rights as defined in FAR 52.227-14 (June 1987) or DFAR 252.227-7015 (b)(2) (November 1995), as applicable in any technical data.

Portions of this software are licensed by third parties including open source terms and conditions.

For detail information on third party licenses, see

<https://edadocs.software.keysight.com/display/engdoc/Notice>

When measuring a capacitor via a Keysight LCR meter, what is the best circuit mode, Cs or Cp?

Contents

Additional Details:.....	4
Small Capacitance (modeled by (a) in above figure).	4
Large Capacitance (modeled by (b) in above figure)	4

When measuring a capacitor via a Keysight LCR meter, what is the best circuit mode, Cs or Cp?

The following guideline (based upon the expected impedance of the capacitor) should be applied for selecting the circuit mode:


For $|Z| \geq 10k$ Ohms, use the parallel circuit mode (Cp);

For $|Z| \leq 10$ Ohms, use series circuit mode (Cs);

For $10 \text{ Ohms} < |Z| < 10K \text{ Ohms}$, follow the manufacturer's recommendations (if available).

Additional Details:

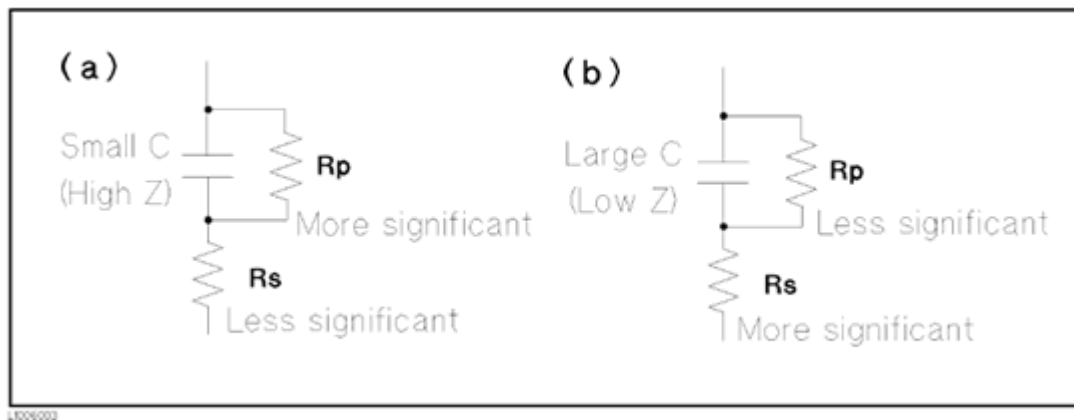To measure L, C, or R, there are two equivalent circuit models. The LCR meter can select the mode by setting the FUNC (function) to Cp, Cs, Lp or Ls. To determine which mode is best, consider the relative impedance magnitude of the reactance, Rs and Rp.



Small Capacitance (modeled by (a) in above figure).

Small capacitance yields large reactance which implies that the effect of the parallel resistance (Rp) has relatively more significance than that of series resistance (Rs). The low value of resistance represented by Rs has negligible significance compared with the capacitive reactance so the parallel circuit mode (Cp-D or Cp-G) should be used.

Large Capacitance (modeled by (b) in above figure)

When the measurement involves a large capacitance (low impedance), Rs has relatively more significance than Rp. The series circuit mode (Cs-D or Cs-Q) should be utilized.

Note that the same concepts apply to inductor measurement as well.

When measuring a capacitor via a Keysight LCR meter, what is the best circuit mode, Cs or Cp?

Learn more about Keysight [LCR Meter and Impedance Measurement](#) products

